

*Lab Assignments for the subject*

## **EMBEDDED SYSTEMS DESIGN (UCS704)**

Submitted by:

Gurjot Singh (102203582)

Anil Kumar (102383026)

Simarpreet Singh (102203606)

Archita Jain (102203613)

Course Instructor(s):

**LECTURE FACULTY: Dr. Deepshikha Tiwari**

**LAB FACULTY: Dr. Shailendra Tiwari**



**THAPAR INSTITUTE OF ENGINEERING AND  
TECHNOLOGY, PATIALA**

Session: July-December 2025

## INDEX

<b>Sr. No.</b>	<b>Title of Experiment</b>	<b>Page No.</b>
1	Truth Table and Logic Gates	3
2	Half Adder	5
3	Full Adder	7
4	Half Subtractor	9
5	Number Converter	11
6	Multiplexer	13
7	Demultiplexer	15
8	Decoder	17
9	Encoder	19
10	D Flip-Flops	21
11	JK Flip Flops	27
12	Counter	29

## Experiment 1 (Truth Table and Logic Gates)

To Study and verify the truth table of various logic gates (NOT,NAND,EX-OR,EX-NOR).

Code:

```
// Logic module
```

```
module ml (A, B, C, D, E, F, G, H, I);
```

```
    input A, B;
```

```
    output C, D, E, F, G, H, I;
```

```
    assign C = A & B;    // AND
```

```
    assign D = A | B;    // OR
```

```
    assign E = A ^ B;    // XOR
```

```
    assign F = ~(A & B); // NAND
```

```
    assign G = ~(A | B); // NOR
```

```
    assign H = ~(A ^ B); // XNOR
```

```
    assign I = ~A;       // NOT A
```

```
endmodule
```

```
// Testbench
```

```
module test;
```

```
    reg a, b;
```

```
    wire c, d, e, f, g, h, i;
```

```
    ml m1(a, b, c, d, e, f, g, h, i);
```

```
    initial begin
```

```

$dumpfile("first.vcd");

$dumpvars(0, test);


$display("A B | AND OR XOR NAND NOR XNOR NOT");
$monitor("%b %b | %b %b %b %b %b %b %b",
        a, b, c, d, e, f, g, h, i);


a = 0; b = 0;
#10 a = 0; b = 1;
#10 a = 1; b = 0;
#10 a = 1; b = 1;
#10 $finish;

end
endmodule

```

### Output:

```

simarpreetsingh@SIMARPREETs-MacBook-Air Coding % vvp ml.out
VCD info: dumpfile first.vcd opened for output.
A B | AND OR XOR NAND NOR XNOR NOT
0 0 | 0 0 0 1 1 1 1
0 1 | 0 1 1 1 0 0 1
1 0 | 0 1 1 1 0 0 0
1 1 | 1 1 0 0 0 1 0
ml.v:35: $finish called at 40 (1s)

```

## Experiment 2 (Half Adder)

To design and verify a half adder using  $S=(X+Y)(X'+Y')$   $C=XY$ .

Code:

```
// Half Adder Module

module half_adder(a, b, carry, sum);

    input a, b;

    output carry, sum;

    assign carry = a & b; // Carry = AND
    assign sum  = a ^ b; // Sum = XOR

endmodule


// Testbench

module test;

    reg a1, b1;

    wire carry1, sum1;

    half_adder H1(a1, b1, carry1, sum1);

    initial begin
        $dumpfile("dump1.vcd");
        $dumpvars(0, test);

        $display("a\tb\tcarry\tsum");
        $monitor("%b\t%b\t %b\t %b", a1, b1, carry1, sum1);

        a1 = 0; b1 = 0;
```

```
#10 a1 = 0; b1 = 1;

#10 a1 = 1; b1 = 0;

#10 a1 = 1; b1 = 1;

#10 $finish;

end

endmodule
```

Output:

```
simarpreetsingh@SIMARPREETs-MacBook-Air Coding % vvp half.out
VCD info: dumpfile dump1.vcd opened for output.
a      b      carry  sum
0      0      0      0
0      1      0      1
1      0      0      1
1      1      1      0
half.v:29: $finish called at 40 (1s)
```

### Experiment 3 (Full Adder)

To design and verify a Full adder using  $S=X'Y'Z+X'YZ'+XY'Z'+XYZ$   
 $C=XY+YZ+XZ$ .

Code:

```
// Full Adder Module
module full_adder(a, b, c, carry, sum);
    input a, b, c;
    output carry, sum;

    assign sum  = a ^ b ^ c;
    assign carry = (a & b) | (b & c) | (a & c);
endmodule

module test;
    reg a1, b1, c1;
    wire carry1, sum1;

    full_adder FA1(a1, b1, c1, carry1, sum1);

    initial begin
        $dumpfile("dump1.vcd");
        $dumpvars(0, test);

        $display("a\tb\tc\tcarry\tsum");
        $monitor("%b\t%b\t%b\t %b\t %b", a1, b1, c1, carry1, sum1);

        a1 = 0; b1 = 0; c1 = 0;
        #10 a1 = 0; b1 = 0; c1 = 1;
```

```
#10 a1 = 0; b1 = 1; c1 = 0;
#10 a1 = 0; b1 = 1; c1 = 1;
#10 a1 = 1; b1 = 0; c1 = 0;
#10 a1 = 1; b1 = 0; c1 = 1;
#10 a1 = 1; b1 = 1; c1 = 0;
#10 a1 = 1; b1 = 1; c1 = 1;
#10 $finish;

end

endmodule
```

Output:

```
simarpreetsingh@SIMARPREETs-MacBook-Air Coding % vvp full.out
VCD info: dumpfile dump1.vcd opened for output.
a      b      c      carry  sum
0      0      0      0      0
0      0      1      0      1
0      1      0      0      1
0      1      1      1      0
1      0      0      0      1
1      0      1      1      0
1      1      0      1      0
1      1      1      1      1
full.v:30: $finish called at 80 (1s)
```



## Experiment 4 (Half Subtractor)

To design and verify a Half Subtractor using  $D=X'Y+XY'$   $B=X'Y$ .

Code:

```
// Half Subtractor Module

module half_sub(a, b, d, bo);

    input a, b;

    output d, bo;

    assign d = a ^ b;

    assign bo = (~a) & b;

endmodule
```

```
module test;

    reg a1, b1;

    wire d1, bo1;


    half_sub HS1(a1, b1, d1, bo1);


    initial begin

        $dumpfile("dump1.vcd");

        $dumpvars(0, test);


        $display("a\tb\tdiff\tborrow");

        $monitor("%b\t%b\t %b\t %b", a1, b1, d1, bo1);


        a1 = 0; b1 = 0;

        #10 a1 = 0; b1 = 1;
```

```
#10 a1 = 1; b1 = 0;

#10 a1 = 1; b1 = 1;

#10 $finish;

end

endmodule
```

Output:

```
simarpreetsingh@SIMARPREETs-MacBook-Air Coding % vvp half_subtractor.out ]
VCD info: dumpfile dump1.vcd opened for output.
a      b      diff      borrow
0      0      0        0
0      1      1        1
1      0      1        0
1      1      0        0
half_subtractor.v:26: $finish called at 40 (1s)
```

## Experiment 5 (Number Converter)

To design a BCD to Excess 3 Code Converter using Combinational Circuits.

Code:

```
// BCD to Ex3 Module
module BCD2Ex3(A, B, C, D, W, X, Y, Z);
    input A, B, C, D;
    output W, X, Y, Z;

    assign W = (A | (B & C)) | (B & D);
    assign X = (A | C) | ((~B) & D) | (B & (~C) & (~D));
    assign Y = ~(C & D);
    assign Z = ~D;
endmodule

module test;
    reg A, B, C, D;
    wire W, X, Y, Z;

    BCD2Ex3 U1(A, B, C, D, W, X, Y, Z);

    initial begin
        $dumpfile("dump_bcd.vcd");
        $dumpvars(0, test);

        $display("A B C D | W X Y Z");
        $monitor("%b %b %b %b | %b %b %b %b",
            A, B, C, D, W, X, Y, Z);
    end
endmodule
```

```

A=0; B=0; C=0; D=0;
#5 A=0; B=0; C=0; D=1;
#5 A=0; B=0; C=1; D=0;
#5 A=0; B=0; C=1; D=1;
#5 A=0; B=1; C=0; D=0;
#5 A=0; B=1; C=0; D=1;
#5 A=0; B=1; C=1; D=0;
#5 A=0; B=1; C=1; D=1;
#5 A=1; B=0; C=0; D=0;
#5 A=1; B=0; C=0; D=1;
#5 $finish;

end

endmodule

```

### Output:

```

simarpreetsingh@SIMARPREETs-MacBook-Air Coding % vvp bcd_ex3.out
VCD info: dumpfile dump_bcd.vcd opened for output.
A B C D | W X Y Z
0 0 0 0 | 0 0 1 1
0 0 0 1 | 0 1 1 0
0 0 1 0 | 0 1 1 1
0 0 1 1 | 0 1 0 0
0 1 0 0 | 0 1 1 1
0 1 0 1 | 1 0 1 0
0 1 1 0 | 1 1 1 1
0 1 1 1 | 1 1 0 0
1 0 0 0 | 1 1 1 1
1 0 0 1 | 1 1 1 0
bcd_ex3.v:35: $finish called at 50 (1s)

```

## Experiment 6 (Multiplexer)

To design and implement a 4:1 Multiplexer.

Code:

```
// 4:1 Multiplexer
```

```
module mux4(s1, s2, a, b, c, d, y);
```

```
input s1, s2, a, b, c, d;
```

```
output y;
```

```
assign y = (~s1 & ~s2 & a) |
```

```
        (~s1 & s2 & b) |
```

```
        ( s1 & ~s2 & c) |
```

```
        ( s1 & s2 & d);
```

```
endmodule
```

```
module testbench;
```

```
reg a, b, c, d, s1, s2;
```

```
wire y;
```

```
mux4 M1(s1, s2, a, b, c, d, y);
```

```
initial begin
```

```
    $dumpfile("mux.vcd");
```

```
    $dumpvars(0, testbench);
```

```
    $display("s1 s2 | a b c d | y");
```

```
    $monitor("%b %b | %b %b %b %b | %b", s1, s2, a, b, c, d, y);
```

```

a=0; b=0; c=0; d=0; s1=0; s2=0;
#10 a=0; b=0; c=0; d=1; s1=0; s2=1;
#10 a=0; b=0; c=1; d=0; s1=1; s2=0;
#10 a=0; b=0; c=1; d=1; s1=1; s2=1;
#10 a=0; b=1; c=0; d=0; s1=0; s2=1;
#10 a=0; b=1; c=0; d=1; s1=1; s2=0;
#10 a=0; b=1; c=1; d=0; s1=1; s2=1;
#10 a=1; b=0; c=0; d=0; s1=1; s2=0;
#10 a=1; b=0; c=0; d=1; s1=1; s2=1;
#10 $finish;

end

endmodule

```

Output:

```

simarpreet Singh@SIMARPREETS-MacBook-Air Coding % vvp mux4.out
VCD info: dumpfile mux.vcd opened for output.
s1 s2 | a b c d | y
0 0 | 0 0 0 0 | 0
0 1 | 0 0 0 1 | 0
1 0 | 0 0 1 0 | 1
1 1 | 0 0 1 1 | 1
0 1 | 0 1 0 0 | 1
1 0 | 0 1 0 1 | 0
1 1 | 0 1 1 0 | 0
1 0 | 1 0 0 0 | 0
1 1 | 1 0 0 1 | 1
mux4.v:33: $finish called at 90 (1s)

```

## Experiment 7 (Demultiplexer)

To design and implement a 1:4 demultiplexer.

Code:

```
module demux(s1,s0,a,b,c,d,e,i);
    input s1,s0,e,i;
    output a,b,c,d;
    assign a =i&e&~s1&~s0;
    assign b =i&e&~s1&s0;
    assign c =i&e&s1&~s0;
    assign d =i&e&s1&s0;
endmodule

module test;
    reg s1, s0, e, i;
    wire a, b, c, d;
    demux obj(s1,s0,a,b,c,d,e,i);
    initial
        begin
            //$dumpfile("demux.vcd");
            //$dumpvars(0, test);
            $display("e\t s1\t s0\t d\t c\t b\t a");
            $monitor("%b\t %b\t %b\t %b\t %b\t %b\t %b" ,e,s1,s0,d,c,b,a);
            i=1; e=0; s1=0; s0=0;
            #10 i=1; e=1; s1=0; s0=0;
            #10 i=1; e=1; s1=0; s0=1;
            #10 i=1; e=1; s1=1; s0=0;
            #10 i=1; e=1; s1=1; s0=1;
            //$finish;
```

```
        end  
    endmodule
```

Output:

```
C:\Users\revol\Desktop\codes>vvp 7.vvp  
e      s1      s0      d      c      b      a  
0      0      0      0      0      0      0  
1      0      0      0      0      0      1  
1      0      1      0      0      1      0  
1      1      0      0      1      0      0  
1      1      1      1      0      0      0
```



## Experiment 8 (Decoder)

To design and verify a 2:4 decoder.

Code:

```
module decoder(a,b,c,d,e,f,E);
    input a,b,E;
    output c,d,e,f;
    assign c = E&a&b;
    assign d = E&a&(~b);
    assign e = E&(~a)&b;
    assign f = E&(~a)&(~b);
endmodule

module testbench;
    reg a, b, E;
    wire c,d,e,f;
    decoder obj(a,b,c,d,e,f,E);
    initial begin
        $display("Inputs    | Outputs");
        $display("E a b | c d e f");
        $monitor("%b %b %b | %b %b %b %b",E,a,b,c,d,e,f);
        E=0 ; a=0; b=0;
        #5 E=1; a=0; b=0;
        #5 E=1; a=0; b=1;
        #5 E=1; a=1; b=0;
        #5 E=1; a=1; b=1;
        #5    $finish;
    end
endmodule
```

Output:

```
C:\Users\revol\Desktop\v codes>vvp 8.vvp
Inputs      |  Outputs
E  a  b    |  c  d  e  f
0  0  0    |  0  0  0  0
1  0  0    |  0  0  0  1
1  0  1    |  0  0  1  0
1  1  0    |  0  1  0  0
1  1  1    |  1  0  0  0
```

## Experiment 9 (Encoder)

To design and implement a 4:2 encoder.

Code:

```
module encoder(a,b,c,d,p,q);
    input a,b,c,d;
    output p,q;
    assign p = a | b;
    assign q = a | c;
endmodule

module test;
    reg a, b, c, d;
    wire p,q;
    encoder obj(a,b,c,d,p,q);
    initial begin

        $display("Inputs    | Outputs");
        $display("A B C D | P Q");
        $monitor("%b %b %b %b | %b %b",a,b,c,d,p,q);
        a=0; b=0; c=0; d=1;
        #5 a=0; b=0; c=1; d=0;
        #5 a=0; b=1; c=0; d=0;
        #5 a=1; b=0; c=0; d=0;

    end
endmodule
```

Output:

```
C:\Users\revol\Desktop\v codes>vvp 9.vvp
Inputs      |  Outputs
A  B  C  D  |  P  Q
0  0  0  1  |  0  0
0  0  1  0  |  0  1
0  1  0  0  |  1  0
1  0  0  0  |  1  1
```

## Experiment 10 (Flip-Flops )

To design and verify the operation of D flip-flops using logic gates.

Code:

(a) D Flip-Flop using NAND GATES

```
module dff_from_nand();
wire Q,Q_BAR;
reg D,CLK;
nand U1 (X,D,CLK) ;
nand U2 (Y,X,CLK) ;
nand U3 (Q,Q_BAR,X);
nand U4 (Q_BAR,Q,Y);
// Testbench
initial begin
    $monitor("CLK = %b D = %b Q = %b Q_BAR = %b",CLK, D, Q, Q_BAR);
    CLK = 0;
    D = 0;
    #3 D = 1;
    #3 D = 0;
    #3 $finish;
end
always #2 CLK = ~CLK;
endmodule
```

Output:

```
C:\Users\revol\Desktop\v codes>vvp 10a.vvp
CLK = 0 D = 0 Q = x Q_BAR = x
CLK = 1 D = 0 Q = 0 Q_BAR = 1
CLK = 1 D = 1 Q = 1 Q_BAR = 0
CLK = 0 D = 1 Q = 1 Q_BAR = 0
CLK = 1 D = 0 Q = 0 Q_BAR = 1
CLK = 0 D = 0 Q = 0 Q_BAR = 1
```

(b) D flip flop with Asynchronous Reset

Code:

```
module Adff(d, rstn, clk, q);
    input d, rstn, clk;
    output reg q;

    always @(posedge clk or negedge rstn) begin
        if (!rstn)
            q <= 0;
        else
            q <= d;
        end
    endmodule
```

```
module tv_dff;
    reg d, rstn, clk;
    wire q;

    Adff obj(d, rstn, clk, q);
```

```
always #10 clk = ~clk;
```

```
initial begin
```

```
    $display(" T\treset \t clk \t D \t| q");
```

```
    $monitor(" %0t \t %d \t %d \t %d | %d",
```

```
        $time, rstn, clk, d, q);
```

```
end
```

```
integer i;
```

```
initial begin
```

```
    clk = 0;
```

```
    d = 0;
```

```
    rstn = 0;
```

```
    #5 rstn = 1;
```

```
    repeat (6) begin
```

```
        d = $urandom_range(0,1);
```

```
        #5;
```

```
    end
```

```
    rstn = 0;
```

```
    repeat (6) begin
```

```
        d = $urandom_range(0,1);
```

```
        #5;
```


```
    end
```

```
    $finish;
```

```
end
```

endmodule

Output:

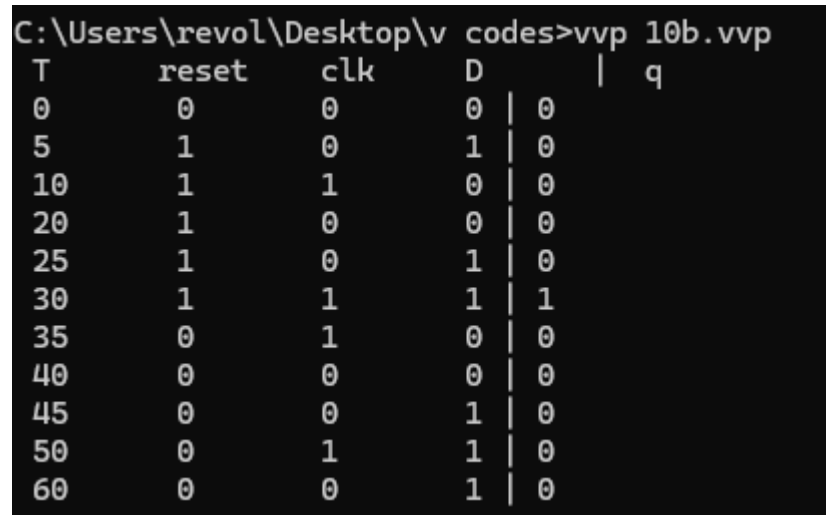

T	reset	clk	D	q
0	0	0	0	0
5	1	0	1	0
10	1	1	0	0
20	1	0	0	0
25	1	0	1	0
30	1	1	1	1
35	0	1	0	0
40	0	0	0	0
45	0	0	1	0
50	0	1	1	0
60	0	0	1	0

(c) D flip flop with synchronous Reset

Code:

```
module Sdff(d, rstn, clk, q);  
    input d, rstn, clk;  
    output reg q;  
  
    always @(posedge clk) begin  
        if (!rstn)  
            q <= 0;  
        else  
            q <= d;  
        end  
    endmodule
```

```
module tv_dff;  
    reg d, rstn, clk;
```



```
wire q;
```

```
Sdff obj(d, rstn, clk, q);
```

```
always #10 clk = ~clk;
```

```
initial begin
```

```
    $display(" T\treset \t clk \t D \t| q");
```

```
    $monitor(" %0t \t %d \t %d \t %d | %d",
```

```
        $time, rstn, clk, d, q);
```

```
end
```

```
integer i;
```

```
initial begin
```

```
    clk = 0;
```

```
    d = 0;
```

```
    rstn = 0;
```

```
    #5 rstn = 1;
```

```
repeat (6) begin
```

```
    d = $urandom_range(0,1);
```

```
    #5;
```

```
end
```

```
rstn = 0;
```

```
repeat (6) begin
```

```
    d = $urandom_range(0,1);
```

```
    #5;
```

end

\$finish;

end

endmodule

Output:

```
C:\Users\revol\Desktop\codes>vvp 10c.vvp
```

T	reset	clk	D	q
0	0	0	0	x
5	1	0	1	x
10	1	1	0	0
20	1	0	0	0
25	1	0	1	0
30	1	1	1	1
35	0	1	0	1
40	0	0	0	1
45	0	0	1	1
50	0	1	1	0
60	0	0	1	0

## Experiment 11 (Flip-Flops )

To design and verify the operation of JK flip-flops using logic gates.

Code:

```
module jkff(input [1:0] jk, input clk, output q, output qb);
```

```
    reg q, qb;
```

```
    always @(posedge clk) begin
```

```
        case(jk)
```

```
            2'b00: q = q;
```

```
            2'b01: q = 0;
```

```
            2'b10: q = 1;
```

```
            2'b11: q = ~q;
```

```
        endcase
```

```
        qb = ~q;
```

```
    end
```

```
endmodule
```

```
// Testbench for JK FF
```

```
module test;
```

```
    reg [1:0] jk;
```

```
    reg clk;
```

```
    integer i;
```

```
    wire q, qb;
```

```
    jkff ob(jk, clk, q, qb);
```

```
    initial begin
```

```
        $dumpfile("first.vcd");
```

```

$dumpvars(1, test);

$display("time\tclk\tjk1\tjk0\tq\t~q");

$monitor("%0t\t%b\t%b\t%b\t%b\t%b",

        $time, clk, jk[1], jk[0], q, qb);

jk = 2'b00; #10
jk = 2'b01; #10
jk = 2'b10; #10
jk = 2'b11; #10

$finish;

end

initial begin
    clk = 0;
    for (i = 0; i <= 20; i = i + 1)
        #5 clk = ~clk;
    end
endmodule

```

### Output:

```

C:\Users\revol\Desktop\v codes>vvp 11.vvp
VCD info: dumpfile first.vcd opened for output.
time      clk      jk1      jk0      q      ~q
0          0        0        0        x        x
5          1        0        0        x        x
10         0        0        1        x        x
15         1        0        1        0        1
20         0        1        0        0        1
25         1        1        0        1        0
30         0        1        1        1        0
35         1        1        1        0        1
40         0        1        1        0        1

```

## Experiment 12 (Counter)

To verify the operation of asynchronous counter.

(a) Up counter

Code:

```
module up_counter(input clk, reset, output [3:0] counter);  
    reg [3:0] counter_up;
```

```
    always @(posedge clk or posedge reset) begin
```

```
        if (reset)
```

```
            counter_up <= 4'd0;
```

```
        else
```

```
            counter_up <= counter_up + 4'd1;
```

```
    end
```

```
    assign counter = counter_up;
```

```
endmodule
```

```
module upcounter_testbench;
```

```
    reg clk, reset;
```

```
    wire [3:0] counter;
```

```
    integer a;
```

```
    up_counter dut(clk, reset, counter);
```

```
    initial begin
```

```
        clk = 0;
```

```
        for (a = 0; a < 10; a = a + 1)
```

```
            #10 clk = ~clk;
```

end

initial begin

\$display("time\tclk\treset\tcounter");

\$monitor("%0t\t%b\t%b\t%b", \$time, clk, reset, counter);

reset = 1;


#20

reset = 0;

end

endmodule

Output:

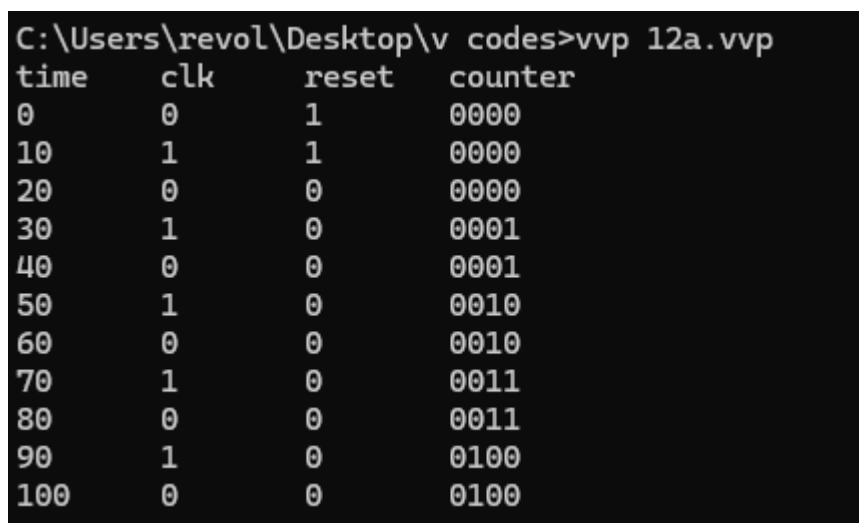

time	clk	reset	counter
0	0	1	0000
10	1	1	0000
20	0	0	0000
30	1	0	0001
40	0	0	0001
50	1	0	0010
60	0	0	0010
70	1	0	0011
80	0	0	0011
90	1	0	0100
100	0	0	0100

(b) Updown counter

Code:

module up\_down\_counter(input clk, reset, up\_down, output [3:0] counter);

reg [3:0] counter\_up\_down;

always @(posedge clk or posedge reset) begin

```

    if (reset)
        counter_up_down <= 4'h0;
    else if (~up_down)
        counter_up_down <= counter_up_down + 4'h1;
    else
        counter_up_down <= counter_up_down - 4'h1;
    end

    assign counter = counter_up_down;
endmodule

```

```

module updowncounter_testbench;

    reg clk, reset, up_down;
    wire [3:0] counter;
    integer a;

    up_down_counter dut(clk, reset, up_down, counter);

    initial begin
        clk = 0;
        for (a = 0; a < 10; a = a + 1)
            #10 clk = ~clk;
        end

    initial begin
        $display("time\tclk\treset\tup_down\tcounter");
        $monitor("%0t\t%b\t%b\t%b\t%b",
            $time, clk, reset, up_down, counter);
    end

```

```
    reset = 1;

    up_down = 0;

    #20;

    reset = 0;

    #20;

    up_down = 1;

end

endmodule
```

Output:

```
C:\Users\revol\Desktop\v codes>vvp 12b.vvp
time    clk    reset  up_down counter
0        0      1       0     0000
10       1      1       0     0000
20       0      0       0     0000
30       1      0       0     0001
40       0      0       1     0001
50       1      0       1     0000
60       0      0       1     0000
70       1      0       1     1111
80       0      0       1     1111
90       1      0       1     1110
100      0      0       1     1110
```